

**SVKM's**  
**D. J. Sanghvi College of Engineering**

**Program: B.Tech in Electronics & Telecommunication Engineering**

**Academic Year: 2022**

**Duration: 3 hours**

**Date: 23.01.2023**




**Time: 09:00 am to 12:00 pm**







**Subject: Electrical Network Analysis and Synthesis (Semester III)**





**Marks: 75**

**Instructions: Candidates should read carefully the instructions printed on the question paper and on the cover page of the Answer Book, which is provided for their use.**

- (1) This question paper contains three pages.**
- (2) Use of Non- Programmable Scientific Calculator.**
- (3) All Questions Are Compulsory.**
- (4) All questions carry equal marks.**
- (5) Answer to each new question is to be started on a fresh page.**
- (6) Figures in the brackets on the right indicate full marks.**
- (7) Assume suitable data wherever required, but justify it.**
- (8) Draw the neat labelled diagrams, wherever necessary.**

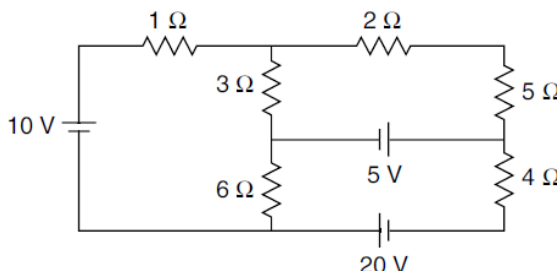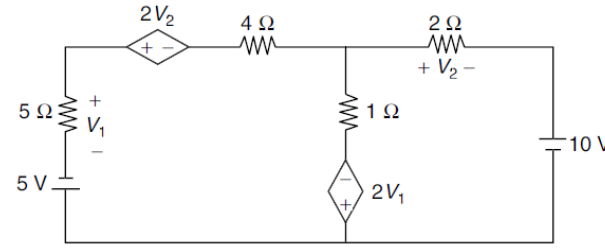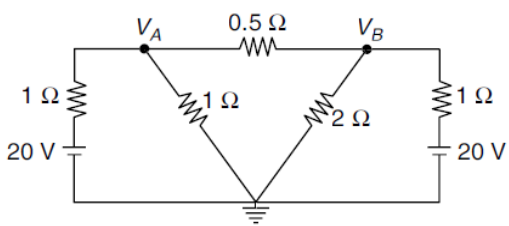Question No.		Max. Marks
Q1 (a)	<p>Using Mesh Analysis, Find the current through 5 Ohm.</p>  <p style="text-align: center;"><b><u>OR</u></b></p> <p>Find Mesh Currents in the network given-</p> 	<p>[05]</p> <p>[05]</p>
Q1 (b)	<p>i. Find the Node Voltages <math>V_A</math> &amp; <math>V_B</math></p> 	[05]

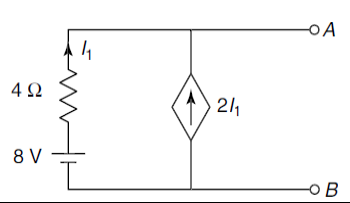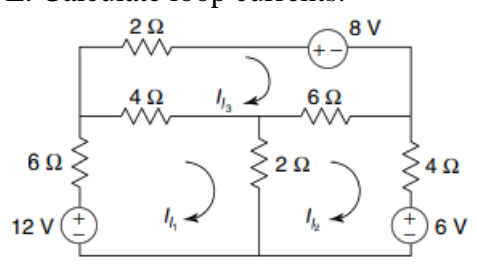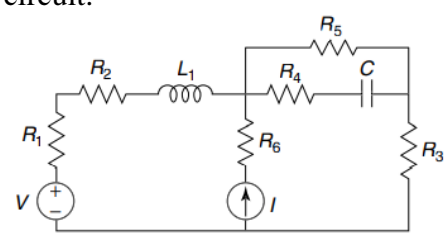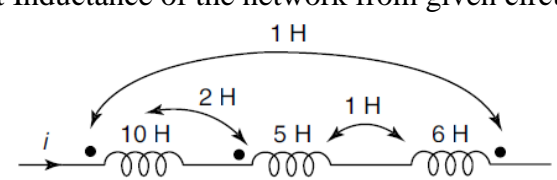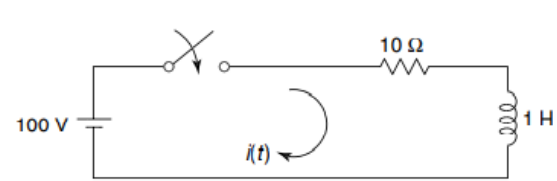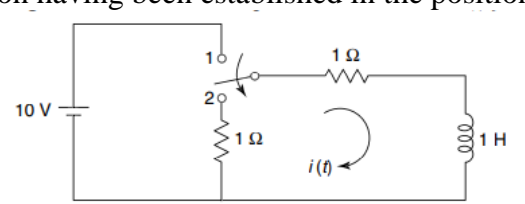	<p>ii. Obtained Thevenin's Equivalent network from the given network at terminal A &amp; B.</p> 	[05]
Q2 (a)	<p>i. Write down the Tieset matrix and obtain the network equilibrium equation in matrix form using KVL. Calculate loop currents.</p>  <p style="text-align: center;"><b>OR</b></p> <p>i. Draw the Oriented graph and Find the Incidence matrix, Also Write down the Tieset matrix of given circuit.</p> 	[10]
Q2 (b)	<p>Find the Equivalent Inductance of the network from given circuit.</p> 	[05]
Q3 (a)	<p>In the given network, the switch is closed at <math>t = 0</math>. With zero current in the inductor, find, <math>i</math>, <math>\frac{di}{dt}</math> and <math>\frac{d^2i}{dt^2}</math> at <math>t=0^+</math></p> 	[05]
Q3 (b)	<p>i. In the network given the switch is moved from the position 1 to 2 at <math>t = 0</math>, steady-state condition having been established in the position 1. Determine <math>i(t)</math></p> 	[05]

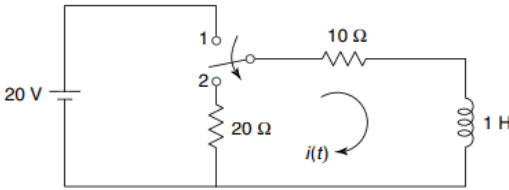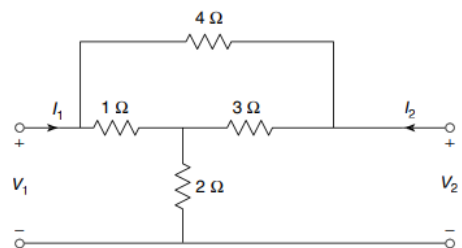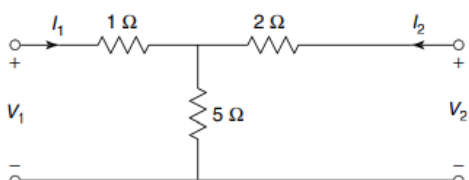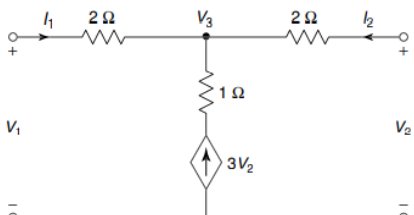	<p>ii) In the network shown, the switch is changed from the position 1 to the position 2 at <math>t = 0</math>, steady condition having reached before switching. Find <math>i</math>, <math>\frac{di}{dt}</math> and <math>\frac{d^2i}{dt^2}</math> at <math>t=0^+</math></p> 	[05]
Q4 (a)	<p>Realise following Impedance function in Foster-I and Foster-II form.</p> $Z(S) = \frac{4(S^2 + 1)(S^2 + 9)}{S(S^2 + 4)}$	[10]
Q4 (b)	<p>i. Test whether given function is Positive Real Function,</p> $F(S) = \frac{(S^2 + 6S + 5)}{(S^2 + 9S + 14)}$ <p><b>OR</b></p> <p>ii. Test whether the given polynomial is Hurwitz or Not?</p> <ol style="list-style-type: none"> <li><math>P(S) = S^3 + 4S^2 + 5S + 2</math></li> <li><math>P(S) = S^4 + 7S^3 + 6S^2 + 21S + 8</math></li> </ol>	[05]
Q5 (a)	<p>i. Find the open-circuit impedance parameters for the given network-</p>  <p>ii. Find the transmission parameters for the given network-</p> 	[05]
Q5 (b)	<p>Find Y-parameters of the given network –</p> 	[05]