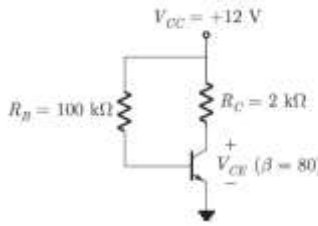
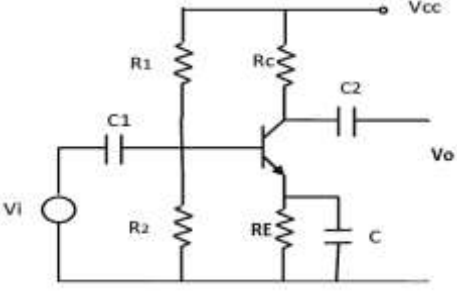
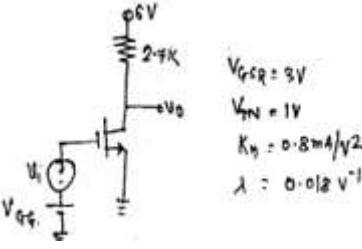
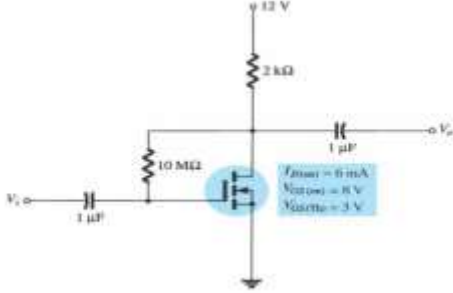
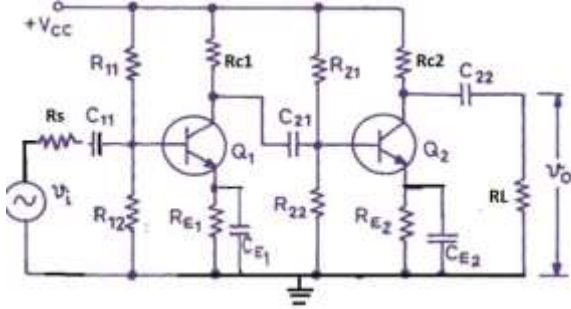
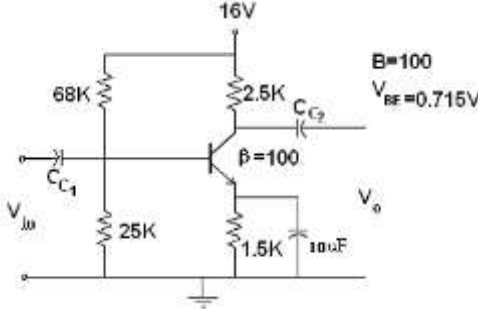


Instructions: Candidates should read carefully the instructions printed on the question paper and on the cover page of the Answer Book, which is provided for their use.

- (1) This question paper contains two pages.
- (2) **All Questions are Compulsory.**
- (3) All questions carry equal marks.
- (4) **Answer to each new question is to be started on a fresh page.**
- (5) **Figures in the brackets on the right indicate full marks.**
- (6) **Assume suitable data wherever required, but justify it.**
- (7) Draw the neat labelled diagrams, wherever necessary.

Question No.		Max. Marks
Q1 (a)	<p>The biasing circuit of a silicon transistor is shown below fig.1. Determine I_C, V_{CE}, V_C and V_B for the transistor?</p>  <p style="text-align: center;">Fig.1</p>	[05]
Q1 (a)	<p style="text-align: center;">OR</p> <p>Draw and explain DC load line of Common emitter amplifier. Why Q point should be at the middle of DC load line and stable ?</p>	[05]
Q1 (b)	<p>i. What are the factors that affect the stability of an amplifier?</p> <p>ii. Explain different types of coupling methods used in multistage amplifiers</p>	[05] [05]

Q2 (a)	<p>For the given circuit shown in fig.2: the circuit and transistor parameters are: $R_1=100k$, $R_2=33k$, $R_c=2k$, $R_E=1k$, $V_{cc}=18V$, $\beta=200$, $V_A= 100V$, $V_{BE}= 0.7V$. Determine</p> <ol style="list-style-type: none"> Q point Hybrid pi model parameters. Small signal voltage gain and input impedance.  <p style="text-align: center;">Fig 2</p> <p style="text-align: center;">OR</p>	[10]
Q2 (a)	<ol style="list-style-type: none"> Describe the biasing for MOSFET. For the circuit shown in fig.3 Draw small signal model and Determine g_m, r_o, Voltage gain, Input impedance and output impedance.  <p style="text-align: center;">Fig.3</p>	[05] [05]
Q2 (b)	Derive expression for Direct coupled Class A power Amplifier	[05]
Q3 (a)	<ol style="list-style-type: none"> Compare D-MOSFET with E-MOSFET. Compare Class A, Class B, Class AB & Class C power amplifiers. 	[05] [05]
Q3 (b)	Explain Wein bridge Oscillator with its advantages and disadvantages.	[05]
Q3 (b)	<p style="text-align: center;">OR</p> <p>Determine I_{DQ} and V_{DSQ} for the given circuit below fig. 4</p>  <p style="text-align: center;">Fig. 4</p>	[05]

Q4 (a)	<p>Calculate the lower 3db frequency (f_L) for the BJT amplifier shown in fig.5 below. Amplifier parameters are: $C_{\pi 1}=C_{\pi 2}=15\text{pF}$, $C_{\mu 1}=C_{\mu 2}=1\text{pF}$, $g_{m1}=g_{m2}=50\text{mA/V}$, $R_s=100\Omega$, $\beta_1=100$, $\beta_2=150$, $r_{\pi 1}=r_{\pi 2}=1.3\text{K}\Omega$, $C_{11}=10\mu\text{F}$, $C_{21}=5\mu\text{F}$, $C_{22}=10\mu\text{F}$, $C_{E1}=C_{E2}=50\mu\text{F}$, $R_{11}=R_{21}=22\text{K}\Omega$, $R_{12}=R_{22}=47\text{K}\Omega$, $R_{c1}=R_{c2}=8.2\text{K}\Omega$, $R_{E1}=R_{E2}=5\text{K}\Omega$, $R_L=5\text{K}\Omega$.</p>  <p style="text-align: right;">Fig.5</p>	[08]
Q4 (a)	<p style="text-align: center;">OR</p> <p>Draw Cascode amplifier using Bipolar Junction Transistor and derive the expression for Q point, overall voltage gain, input impedance and output impedance.</p>	[08]
Q4 (b)	<p>For the circuit shown in fig. 6 determine the I_{CQ}, V_{CEQ}, V_E, V_C, V_B and small signal voltage gain. Also plot the DC load line and locate Q-point.</p> 	[07]
Q5 (a)	<p>Write a short note on- (Attempt any two.)</p> <ul style="list-style-type: none"> i) Barkhausen's criteria to sustained oscillation ii) Cross Over Distortion of power amplifier. iii) Darlington emitter follower. iv) Frequency response of RC coupled amplifier. 	<p>[05]</p> <p>[05]</p> <p>[05]</p> <p>[05]</p>
Q5 (b)	<p>Explain Different topologies of negative feedback amplifiers.</p>	[05]

All the Best!